


# **Program Assignment 2: Static Timing Analysis**

**TA: 陳維亮(Wei-Liang Chen)**

**Email: [tracelementx@gmail.com](mailto:tracelementx@gmail.com)**

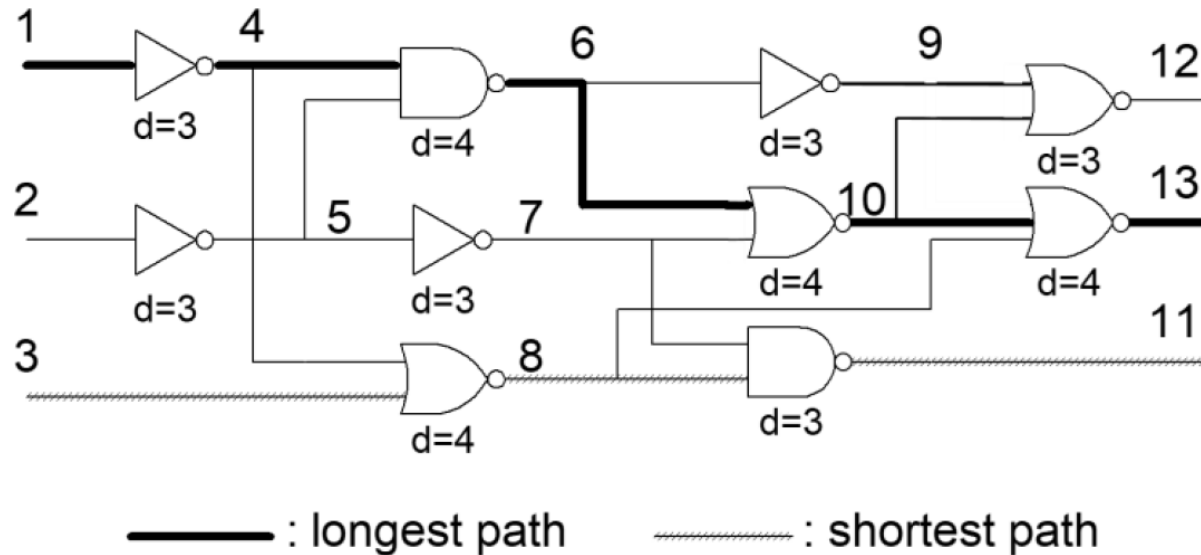
# Delay Calculation

- Given a gate-level netlist
  - Determine propagation delay and output transition time (slew) of each gate
  - Find the longest path and the shortest path


 
# Delay Calculation on a Cell


- Lookup table
  - Table Input
    - Input transition time (slew)
    - Output capacitance
  - Table output
    - Delay
    - Output transition time (slew)



Input Transition (ns)	Total Output Load (fF)				
	0.2	0.3	0.4	0.5	
	0	3	4.5	6	7
	0.1	5	8	10.7	13
Cell Delay (ps)					
 
# Delay Calculation on Multi-input Cell

- Multiple timing arcs (delay and slew) may be found, input transition time is defined by the input that arrives latest



- In this example, signal of input pin “B” will define the input transition time of this gate

# Worst-case Output Calculation

- After you get the input transition time and output loading, calculate the propagation delay of both output situations (output = 0 and output = 1)
- The one that has larger propagation delay will be the worst-case output, then output transition time is defined according to worst-case output
  - If the output is 0, output transition time is defined by its output falling time
  - If the output is 1, output transition time is defined by its output rising time

# Boundary Condition & Assumption

- Input transition time set to **0ns**
- Output loading set to **0.03pF**
- Wire Delay set to **0.005ns**

